### **Assignment 1**

Link to this Assignment

### Part 1

- 1. this repository
- 2. this README.md:
- 3. styles in Markdown:

а	b	С
0	1	0

```
architecture testbench of tb_gates is

-- Local signals
    signal s_a : std_logic;
    signal s_b : std_logic;
    signal s_for : std_logic;
    signal s_fand : std_logic;
    signal s_fxor : std_logic;
```

- unordered list
- test 123

Back to top of repository

## Part 2

### Part 3

### De Morgan's law verification

```
f(c,b,a) = \overline{b}\,a + \overline{c}\,\overline{b}
```

$$f_{NOR}(c, b, a) = \overline{b + \overline{a + a}} + \overline{c + b}$$

$$f_{NAND}(c,b,a) = \overline{\overline{b \cdot b} \cdot a} \ \cdot \ \overline{\overline{c \cdot c} \cdot \overline{b \cdot b}}$$

#### Truth table

С	b	а	f(c,b,a)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0


### Code of architecture

```
architecture dataflow of gates is
begin
    fo_o <= ((not b_i) and a_i) or ((not c_i) and (not b_i));
    fnor_o <= ((b_i nor (a_i nor a_i)) nor (c_i nor b_i)) nor ((b_i nor (a_i nor a_i)) nor (c_i nor b_i));
    fnand_o <= (((b_i nand b_i) nand a_i) nand ((c_i nand c_i) nand (b_i nand b_i)));
end architecture dataflow;</pre>
```

### Playground link

link to playground

### Waveforms screenshot

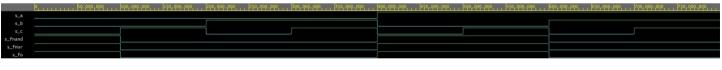

# basic Boolean postulates

### Code of architecture

```
architecture dataflow of gates is
begin
   f1_o <= x_i and not(x_i);
   f2_o <= x_i or not(x_i);
   f3_o <= x_i or x_i or x_i;
   f4_o <= x_i and x_i and x_i;

end architecture dataflow;</pre>
```

### Playground link

link to playground

### Waveforms screenshot

### Distributive laws

### Code of architecture

```
architecture dataflow of gates is
begin
   f1R_o <= (x_i and y_i) or (x_i and z_i);
   f1L_o <= x_i and (y_i or z_i);
   f2R_o <= (x_i or y_i) and (x_i or z_i);
   f2L_o <= x_i or (y_i and z_i);

end architecture dataflow;</pre>
```

## Playground link

link to playground

### Waveforms screenshot